

# Application Note

## AN- EVAL-ICE2QR4765Z

12W5V Evaluation Board with Quasi-Resonant CoolSET<sup>®</sup> ICE2QR4765Z

Power Management & Supply



N e v e r   s t o p   t h i n k i n g .

**Published by**  
**Infineon Technologies AG**  
**81726 Munich, Germany**  
**© 2011 Infineon Technologies AG**  
**All Rights Reserved.**

**Legal Disclaimer**

The information given in this document shall in no event be regarded as a guarantee of conditions or characteristics. With respect to any examples or hints given herein, any typical values stated herein and/or any information regarding the application of the device, Infineon Technologies hereby disclaims any and all warranties and liabilities of any kind, including without limitation, warranties of non-infringement of intellectual property rights of any third party.

**Information**

For further information on technology, delivery terms and conditions and prices, please contact the nearest Infineon Technologies Office ([www.infineon.com](http://www.infineon.com)).

**Warnings**

Due to technical requirements, components may contain dangerous substances. For information on the types in question, please contact the nearest Infineon Technologies Office.

Infineon Technologies components may be used in life-support devices or systems only with the express written approval of Infineon Technologies, if a failure of such components can reasonably be expected to cause the failure of that life-support device or system or to affect the safety or effectiveness of that device or system. Life support devices or systems are intended to be implanted in the human body or to support and/or maintain and sustain and/or protect human life. If they fail, it is reasonable to assume that the health of the user or other persons may be endangered.

---

**Title****Revision History:** 4 August 2011 V1.0

Previous Version: none

Page	Subjects (major changes since last revision)

12W5V Evaluation Board with Quasi-Resonant CoolSET® ICE2QR4765Z  
License to Infineon Technologies Asia Pacific Pte Ltd

AN-PS0064

**Winson Wong**[Winson.wong@infineon.com](mailto:Winson.wong@infineon.com)**Eric Kok**[Eric.kok@infineon.com](mailto:Eric.kok@infineon.com)**We Listen to Your Comments**

Any information within this document that you feel is wrong, unclear or missing at all?  
Your feedback will help us to continuously improve the quality of this document.  
Please send your proposal (including a reference to this document) to:

[comments@infineon.com](mailto:comments@infineon.com)

Table of Contents

1	<b>Content</b> .....	6
2	<b>Evaluation Board</b> .....	6
3	<b>List of Features</b> .....	6
4	<b>Technical Specifications</b> .....	7
5	<b>Circuit Description</b> .....	7
5.1	Mains Input and Rectification .....	7
5.2	Integrated MOSFET and PWM Control.....	7
5.3	Snubber Network .....	7
5.4	Output Stage.....	7
5.5	Feedback Loop.....	7
6	<b>Circuit Operation</b> .....	7
6.1	Startup Operation.....	7
6.2	Normal Mode Operation .....	8
6.3	Primary side peak current control.....	8
6.4	Digital Frequency Reduction .....	8
6.5	Burst Mode Operation .....	8
7	<b>Protection Features</b> .....	8
7.1	Vcc under voltage and over voltage protection.....	8
7.2	Foldback point protection .....	9
7.3	Open loop/over load protection.....	9
7.4	Adjustable output overvoltage protection.....	9
7.5	Short winding protection.....	9
7.6	Auto restart for over temperature protection.....	9
8	<b>Circuit diagram</b> .....	10
8.1	PCB Top overlayer .....	11
8.2	PCB Bottom Layer .....	12
9	<b>Component List</b> .....	13
10	<b>Transformer Construction</b> .....	14
11	<b>Test Results</b> .....	14
11.1	Efficiency and standby performance .....	14
12	<b>Waveform and scope plots</b> .....	16
12.1	Startup @85Vac and 12W load .....	16
12.2	Working at different zero crossing point.....	17
12.3	Load transient response .....	17
12.4	AC Output ripple during full load .....	18
12.5	Burst mode operation.....	18
13	<b>References</b> .....	19

## 1 Content

This application note is a description of 12W switching mode power supply evaluation board designed in a quasi resonant flyback converter topology using ICE2QR4765Z Quasi-resonant CoolSET<sup>®</sup>. The target application of ICE2QR4765Z are for set-top box, portable game controller, DVD player, netbook adapter and auxiliary power supply for LCD TV, etc. With the CoolMOS<sup>®</sup> integrated in this IC, it greatly simplifies the design and layout of the PCB. Due to valley switching, the turn on voltage is reduced and this offers higher conversion efficiency comparing to hard-switching flyback converter. With the DCM mode control, the reverse recovery problem of secondary rectify diode is relieved. And for its natural frequency jittering with line voltage, the EMI performance is better. Infineon's digital frequency reduction technology enables a quasi-resonant operation till very low load. As a result, the system efficiency, over the entire load range, is significantly improved compared to conventional free running quasi resonant converter implemented with only maximum switching frequency limitation at light load. In addition, numerous adjustable protection functions have been implemented in ICE2QR4765Z to protect the system and customize the IC for the chosen application. In case of failure modes, like open control-loop/over load, output overvoltage, and transformer short winding, the device switches into **Auto Restart Mode** or **Latch-off Mode**. By means of the cycle-by-cycle peak current limitation plus foldback point correction, the dimension of the transformer and current rating of the secondary diode can both be optimized. Thus, a cost effective solution can be easily achieved.

## 2 Evaluation Board



Figure 1 EVAL-ICE2QR4765Z-12W

## 3 List of Features

<b>650V</b> avalanche rugged CoolMOS <sup>®</sup> with built in <b>depletion startup cell</b>
<b>Quasi-resonant</b> operation
<b>Digital frequency reduction</b> with decreasing load
Cycle-by-cycle peak current limitation with <b>foldback point correction</b>
Built-in <b>digital soft-start</b>
Direct current sensing with internal <b>Leading Edge Blanking Time</b>
VCC under voltage protection: <b>IC stop operation, recover with softstart</b>
VCC over voltage protection: <b>IC stop operation, recover with softstart</b>
Openloop/Overload protection: <b>Auto Restart</b>
Output overvoltage protection: <b>Latch-off with adjustable threshold</b>
Short-winding protection: <b>Latch-off</b>
Over temperature protection: <b>Autorestart</b>

## 4 Technical Specifications

Input voltage	85Vac~265Vac
Input frequency	50Hz, 60Hz
Output voltage and current	5V 2.4A
Output power	12W
Efficiency	>76% at full load
Standby power	<50mW@no load
Minimum switching frequency at full load, minimum input voltage	65kHz

## 5 Circuit Description

### 5.1 Mains Input and Rectification

The AC line input side comprises the input fuse F1 as overcurrent protection. The X2 Capacitors C1 and Choke L1 form a main filter to minimize the feedback of RFI into the main supply. After the bridge rectifier BR1, together with a smoothing capacitor C2, provide a voltage of 70VDC to 380 VDC depending on mains input voltage.

### 5.2 Integrated MOSFET and PWM Control

ICE2QR4765Z is comprised of a power MOSFET and the quasi-resonant controller; this integrated solution greatly simplifies the circuit layout and reduces the cost of PCB manufacturing. The PWM switch-on is determined by the zero-crossing input signal and the value of the up/down counter. The PWM switch-off is determined by the feedback signal  $V_{FB}$  and the current sensing signal  $V_{CS}$ . ICE2QR4765Z also performs all necessary protection functions in flyback converters. Details about the information mentioned above are illustrated in the product datasheet.

### 5.3 Snubber Network

A snubber network R1, C3 and D1 dissipate the energy of the leakage inductance and suppress ringing on the SMPS transformer.

### 5.4 Output Stage

On the secondary side, 5V output, the power is coupled out via a schottky diode D21. The capacitors C21 provides energy buffering followed by the L-C filters L21 and C22 to reduce the output ripple and prevent interference between SMPS switching frequency and line frequency considerably. Storage capacitors C21 is designed to have an internal resistance (ESR) as small as possible. This is to minimize the output voltage ripple caused by the triangular current.

### 5.5 Feedback Loop

For feedback, the output is sensed by the voltage divider of Rc1 and Rc3 and compared to TL431 internal reference voltage. Cc1, Cc2 and Rc4 comprise the compensation network. The output voltage of TL431 is converted to the current signal via optocoupler IC2 and two resistors Rc5 and Rc6 for regulation control.

## 6 Circuit Operation

### 6.1 Startup Operation

Since there is a built-in startup cell in the ICE2QR4765Z, there is no need for external start up resistor, which can improve standby performance significantly.

When VCC reaches the turn on voltage threshold 18V, the IC begins with a soft start. The soft-start implemented in ICE2QR4765Z is a digital time-based function. The preset soft-start time is 12ms with 4 steps. If not limited by other functions, the peak voltage on CS pin will increase step by step from 0.32V to 1V finally. After IC turns on, the Vcc voltage is supplied by auxiliary windings of the transformer.

## 6.2 Normal Mode Operation

The secondary output voltage is built up after startup. The secondary regulation control is adopted with TL431 and optocoupler. The compensation network Cc1, Cc2 and Rc4 constitute the external circuitry of the error amplifier of TL431. This circuitry allows the feedback to be precisely controlled with respect to dynamically varying load conditions, therefore providing stable control.

## 6.3 Primary side peak current control

The MOSFET drain source current is sensed via external resistor R4 and R4A. Since ICE2QR4765Z is a current mode controller, it would have a cycle-by-cycle primary current and feedback voltage control which can make sure the maximum power of the converter is controlled in every switching cycle.

## 6.4 Digital Frequency Reduction

During normal operation, the switching frequency for ICE2QR4765Z is digitally reduced with decreasing load. At light load, the MOSFET will be turned on not at the first minimum drain-source voltage time, but on the  $n^{\text{th}}$ . The counter is in range of 1 to 7, which depends on feedback voltage in a time-base. The feedback voltage decreases when the output power requirement decreases, and vice versa. Therefore, the counter is set by monitoring voltage  $V_{\text{FB}}$ . The counter will be increased with low  $V_{\text{FB}}$  and decreased with high  $V_{\text{FB}}$ . The thresholds are preset inside the IC.

## 6.5 Burst Mode Operation

At light load condition, the SMPS enters into Active Burst Mode. At this stage, the controller is always active but the Vcc must be kept above the switch off threshold. During active burst mode, the efficiency increase significantly and at the same time it supports low ripple on  $V_{\text{out}}$  and fast response on load jump.

For determination of entering Active Burst Mode operation, three conditions apply:

- .the feedback voltage is lower than the threshold of  $V_{\text{FBEB}}$ (1.25V). Accordingly, the peak current sense voltage across the shunt resistor is 0.18;
- .the up/down counter is 7;
- .and a certain blanking time ( $t_{\text{BEB}}$ ).

Once all of these conditions are fulfilled, the Active Burst Mode flip-flop is set and the controller enters Active Burst Mode operation. This multi-condition determination for entering Active Burst Mode operation prevents mistriggering of entering Active Burst Mode operation, so that the controller enters Active Burst Mode operation only when the output power is really low during the preset blanking time.

During active burst mode, the maximum current sense voltage is reduced from 1V to 0.34V so as to reduce the conduction loss and the audible noise. At the burst mode, the FB voltage is changing like a sawtooth between 3.0 and 3.6V.

The feedback voltage immediately increases if there is a high load jump. This is observed by one comparator. As the current limit is 34% during Active Burst Mode a certain load is needed so that feedback voltage can exceed VLB (4.5V). After leaving active burst mode, maximum current can now be provided to stabilize  $V_{\text{O}}$ . In addition, the up/down counter will be set to 1 immediately after leaving Active Burst Mode. This is helpful to decrease the output voltage undershoot

# 7 Protection Features

## 7.1 Vcc under voltage and over voltage protection

During normal operation, the VCC voltage is continuously monitored. When the Vcc voltage falls below the under voltage lock out level (VCCoff) or the Vcc voltage increases up to VCCovp, the IC will enter into autorestart mode.

## 7.2 Foldback point protection

For a quasi-resonant flyback converter, the maximum possible output power is increased when a constant current limit value is used for all the mains input voltage range. This is usually not desired as this will increase additional cost on transformer and output diode in case of output over power conditions.

The internal fold back protection is implemented to adjust the Vcs voltage limit according to the bus voltage. Here, the input line voltage is sensed using the current flowing out of ZC pin, during the MOSFET on-time. As the result, the maximum current limit will be lower at high input voltage and the maximum output power can be well limited versus the input voltage.

## 7.3 Open loop/over load protection

In case of open control loop, feedback voltage is pulled up with internally block. After a fixed blanking time 30ms, the IC enters into auto restart mode. In case of secondary short-circuit or overload, regulation voltage V<sub>FB</sub> will also be pulled up, same protection is applied and IC will auto restart.

## 7.4 Adjustable output overvoltage protection

During off-time of the power switch, the voltage at the zero-crossing pin ZC is monitored for output overvoltage detection. If the voltage is higher than the preset threshold 3.7V for a preset period 100µs, the IC is latched off.

## 7.5 Short winding protection

The source current of the MOSFET is sensed via two shunt resistors R5 and R5A in parallel. If the voltage at the current sensing pin is higher than the preset threshold V<sub>CSSW</sub> of 1.68V during the on-time of the power switch, the IC is latched off. This constitutes a short winding protection. To avoid an accidental latch off, a spike blanking time of 190ns is integrated in the output of internal comparator.

## 7.6 Auto restart for over temperature protection

The IC has a built-in over temperature protection function. When the controller's temperature reaches 140 °C, the IC will shut down switch and enters into autorestart. This can protect power MOSFET from overheated.



### 8 Circuit diagram

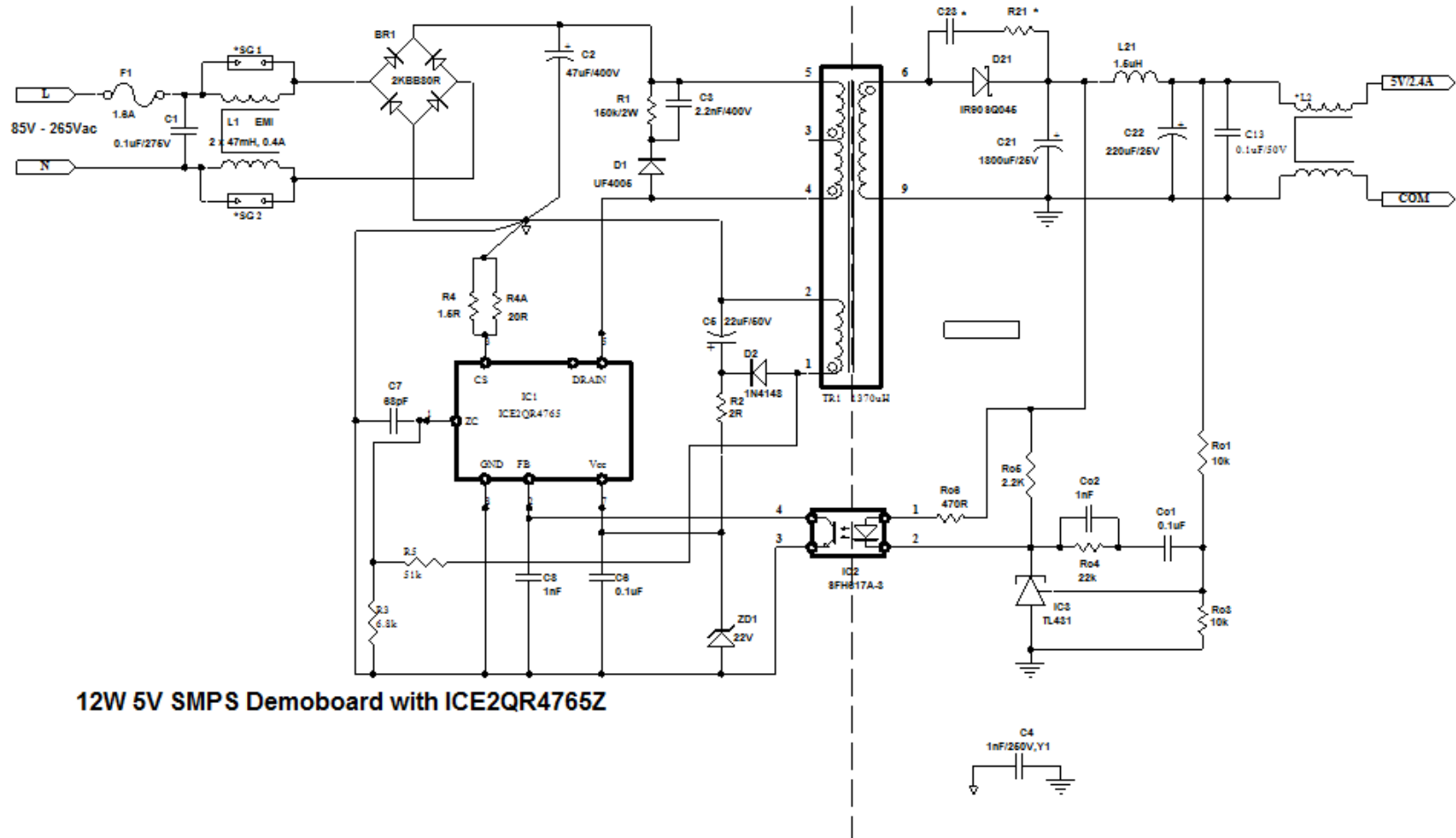


Figure 2 – Schematics

8.1 PCB Top overlay

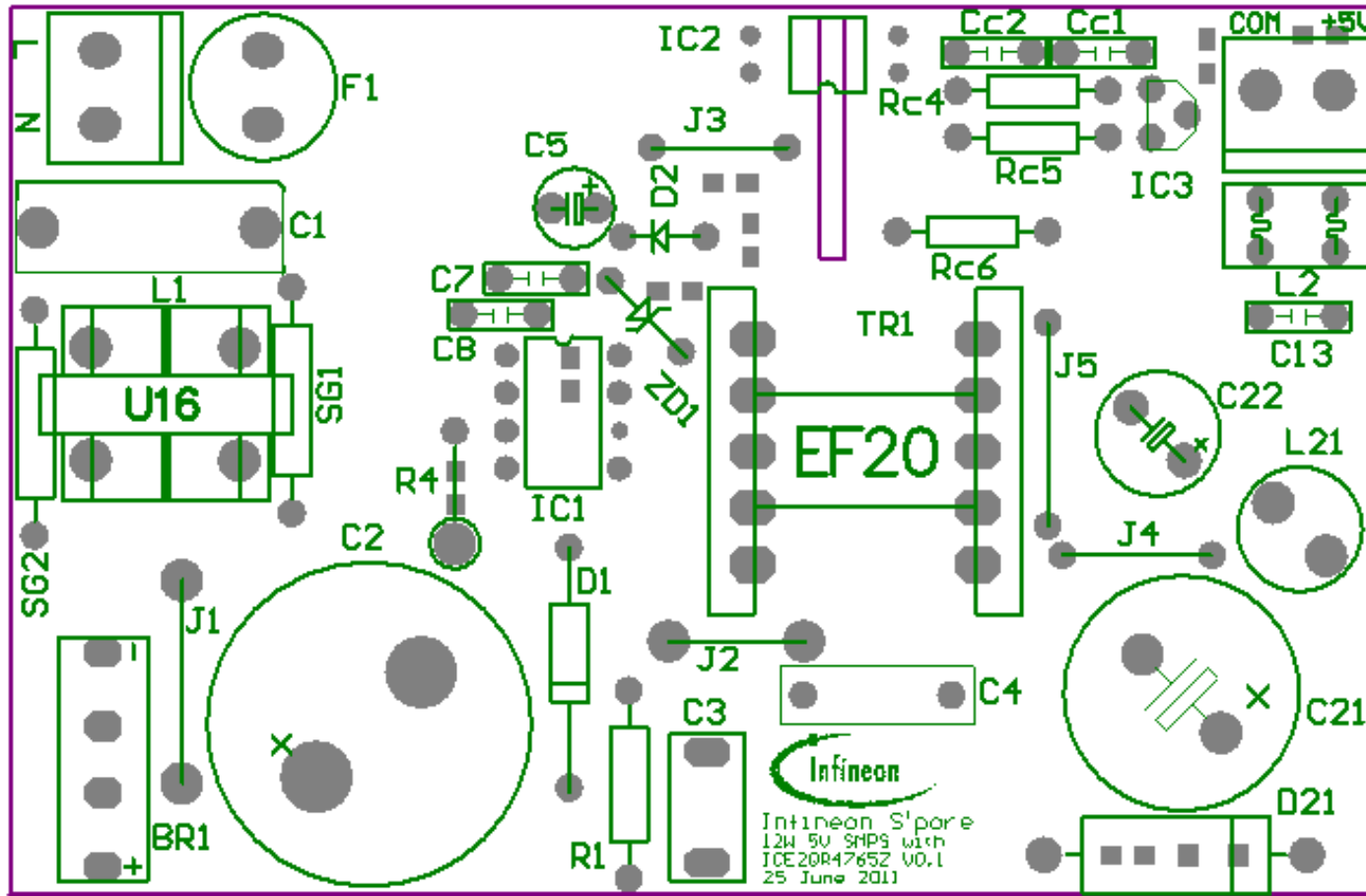


Figure 3 –Component Legend – View from topside

8.2 PCB Bottom Layer

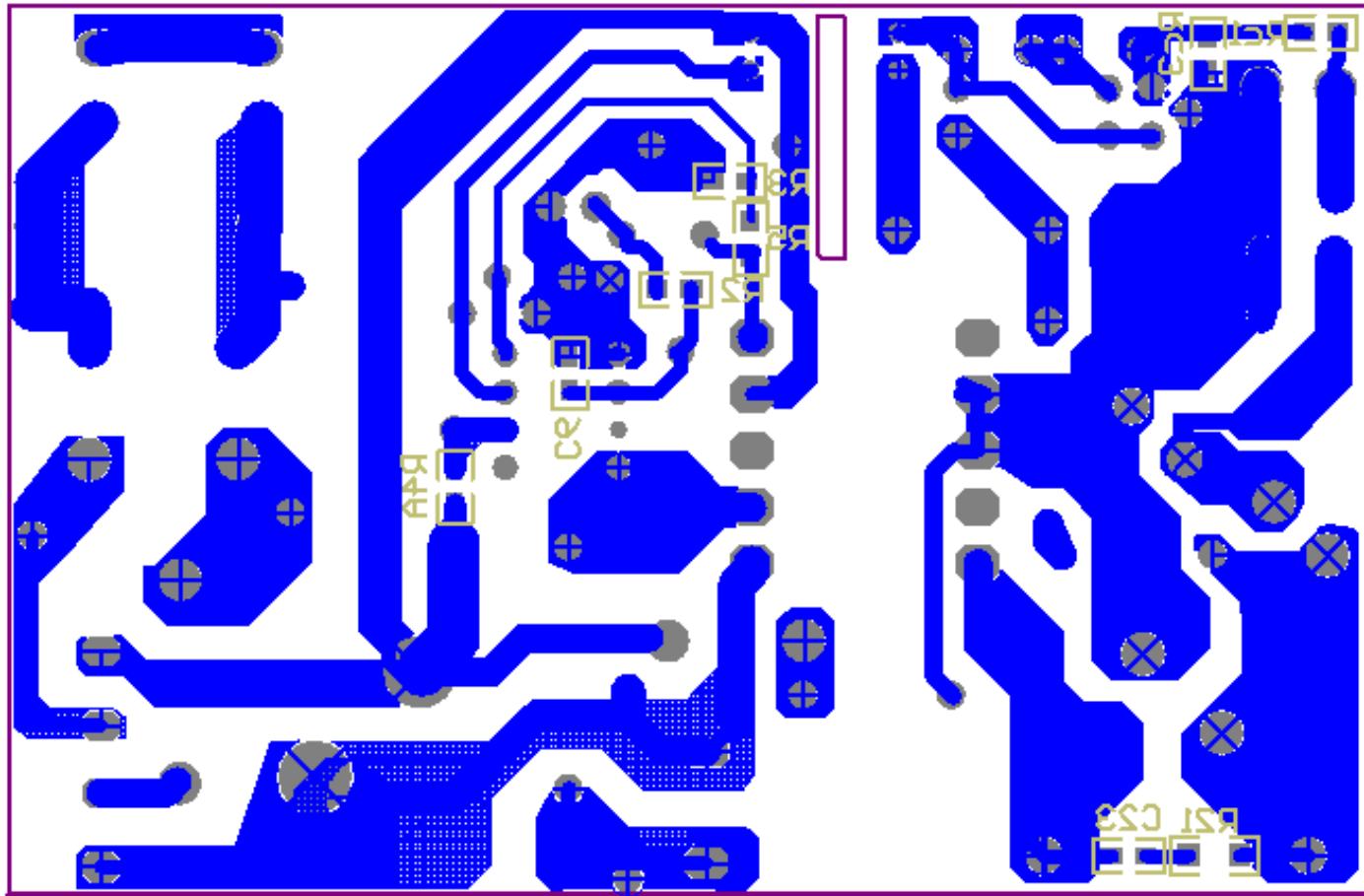


Figure 4 Solder side copper – View from bottom side

## 9 Component List

**Table 1– Component List**

Items	Designator	Part Type	Part No.	Manufacturer
1	BR1	2KBB80R		
2	F1	1.6A/250Vac		
3	L21	1.5uH		
4	R1	150k/2W		
5	R2	2R, SMD		
6	R3	6.8k, SMD		
7	R4	1.5R		
8	R4A	20R, SMD		
9	R5	51k, SMD		
10	Rc1	10k, SMD		
11	Rc3	10k, SMD		
12	Rc4	22k		
13	Rc5	2.2K		
14	Rc6	470R		
15	R21	*		
16	C1	0.1uF/305V	B32922C3104K000	Epcos
17	C2	47uF/400V	B43504A9476M	Epcos
18	C3	2.2nF/630V		
19	C4	1nF/250V,Y1	DE1E3KX102MA4BL01	Murata
20	C5	22uF/50V	B41851A6226M000	Epcos
21	C6	0.1uF, SMD		
22	C7	68pF		
23	C8	1nF		
24	C13	0.1uF/50V	RPER71H104K2K1A03B	Murata
25	C21	1800uF/25V		
26	C22	220uF/25V		
27	Cc1	0.1uF	RPER71H104K2K1A03B	Murata
28	Cc2	1nF		
29	C23	*		
30	EMI	2 x 47mH, 0.4A	B82731R2401A30	Epcos
31	TR1	1370uH		Epcos
32	IC2	SFH617A-3		
33	IC3	TL431		
34	D1	UF4005	UF4005	Vishay
35	D2	1N4148		
36	ZD1	22V zenor diode		
37	D21	IR90SQ045		

## 10 Transformer Construction

Core and material: EF20/10/6, EPCOS N87

Bobbin: Horizontal Version

Primary Inductance,  $L_p=707\mu\text{H}$ , measured between pin 5 and pin 4 (Gapped to Inductance)

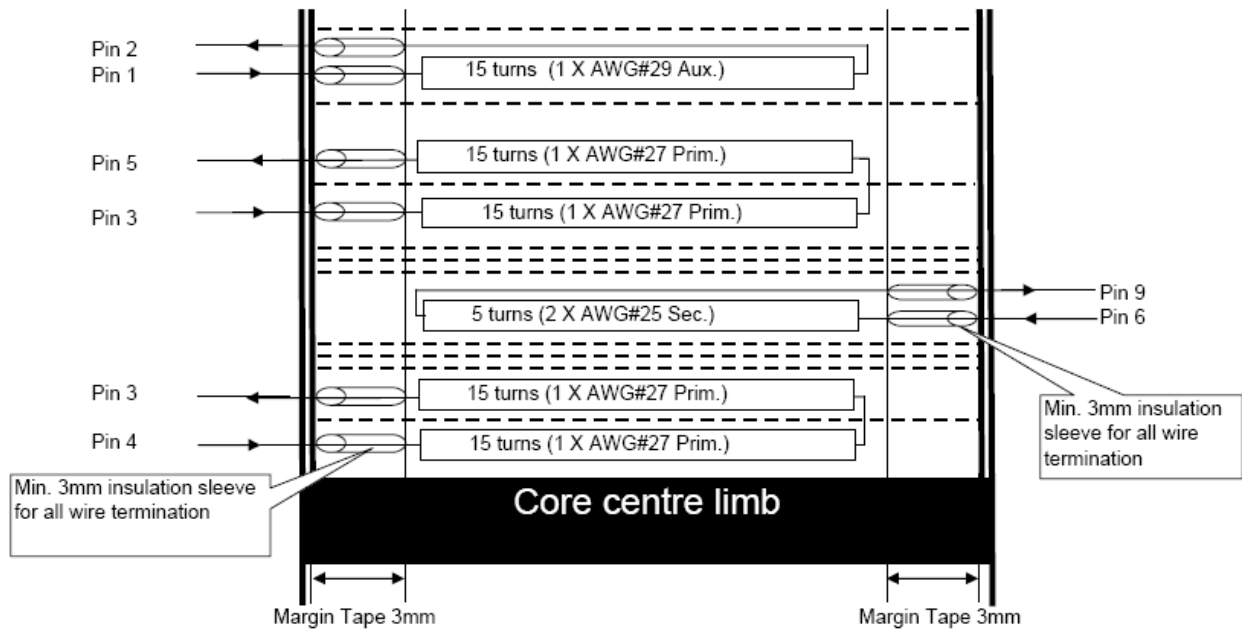


Figure 5 – Transformer structure

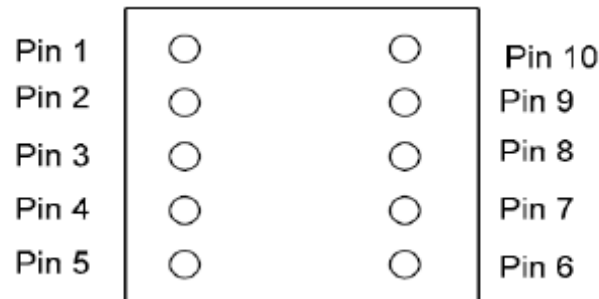


Figure 6 – Transformer complete – top view

Table 2 wire gauge used of the transformer windings

Start	Stop	No. of turns	Wire size	Layer
1	2	15	1XAWG#29	Auxiliary
3	5	30(15+15)	1XAWG#27	$\frac{1}{2}$ Primary
6	9	5	2XAWG#25	Secondary
4	3	30(15+15)	1XAWG#27	$\frac{1}{2}$ Primary

## 11 Test Results

### 11.1 Efficiency and standby performance

Input Voltage (Vac)	Input Power (W)	Vo (V)	Io (A)	Po (W)	Efficiency (%)
85	3.725	4.996	0.6	2.9976	80.47
85	7.59	4.995	1.2	5.994	78.97
85	11.399	4.994	1.8	8.9892	78.86
85	15.679	4.991	2.4	11.9784	76.40
115	3.715	4.996	0.6	2.9976	80.69
115	7.44	4.995	1.2	5.994	80.56
115	11.156	4.994	1.8	8.9892	80.58
115	15.126	4.993	2.4	11.9832	79.22
230	3.79	4.995	0.6	2.997	79.08
230	7.499	4.995	1.2	5.994	79.93
230	11.206	4.993	1.8	8.9874	80.20
230	14.79	4.992	2.4	11.9808	81.01

Table 3 – Efficiency vs. Load

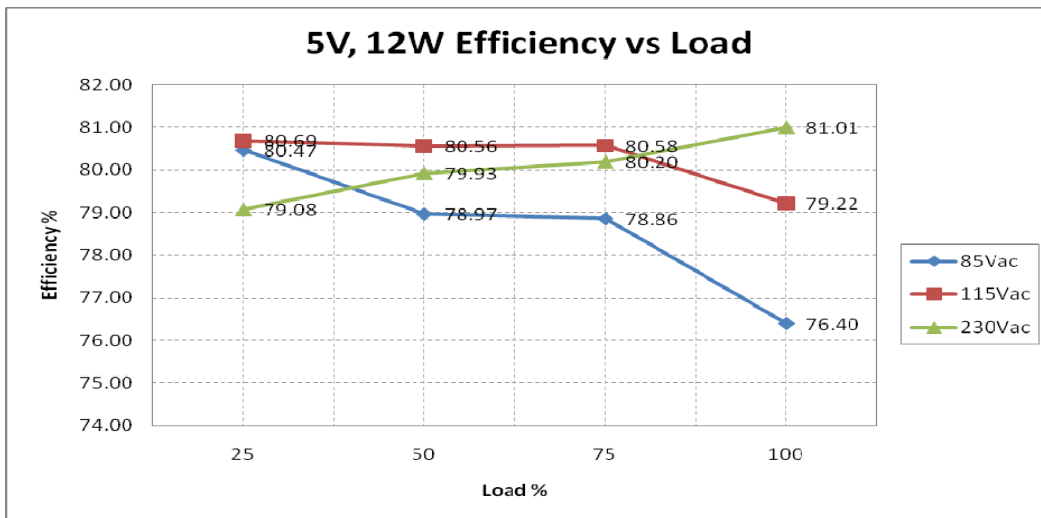


Figure 7 – Efficiency vs. Load

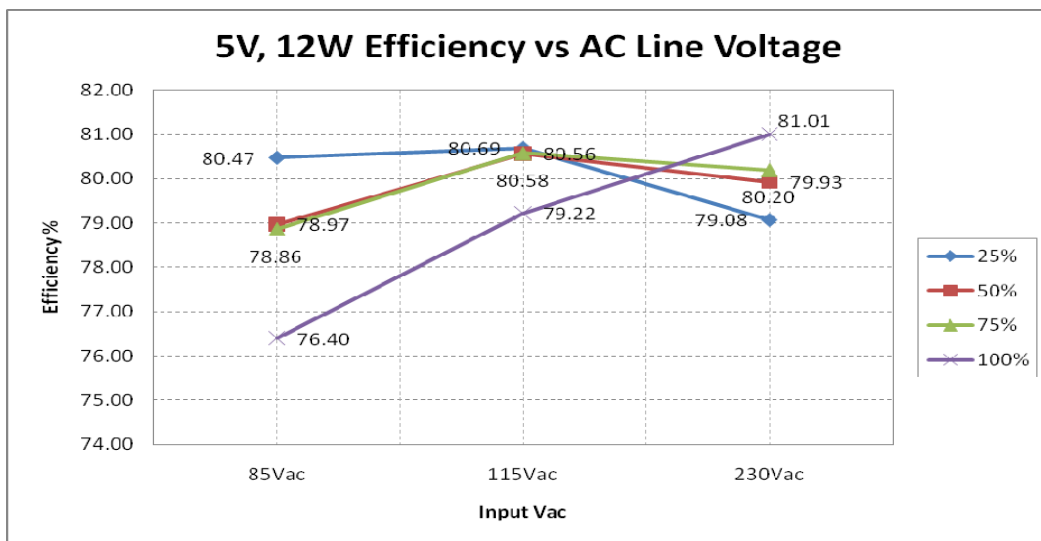


Figure 8 Efficiency vs AC line voltage

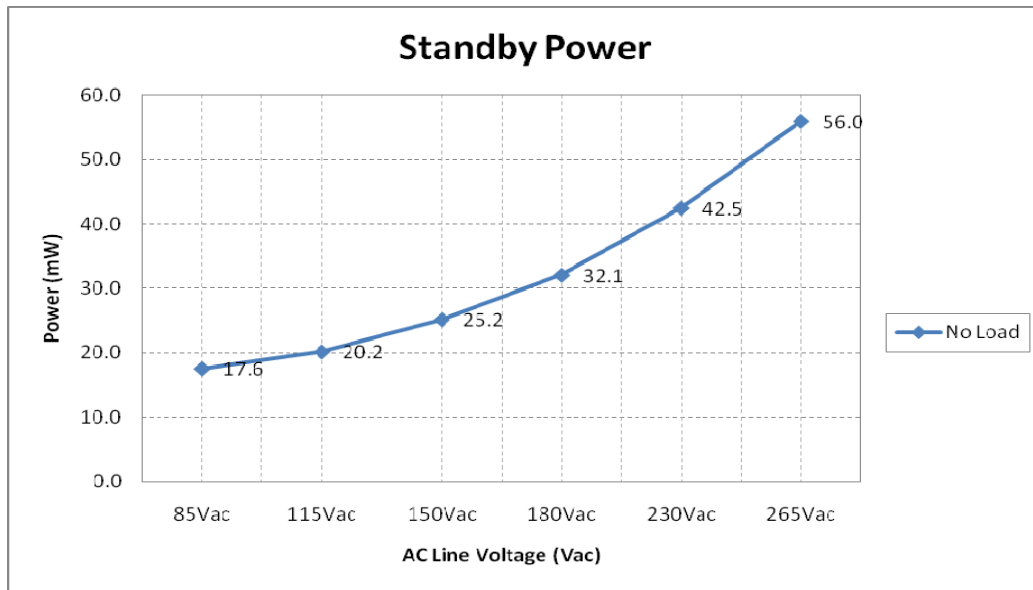


Figure 9 Standby Power vs AC line voltage

## 12 Waveform and scope plots

All waveform and scope were recorded with LeCroy 44Xi oscilloscope.

### 12.1 Startup @85Vac and 12W load

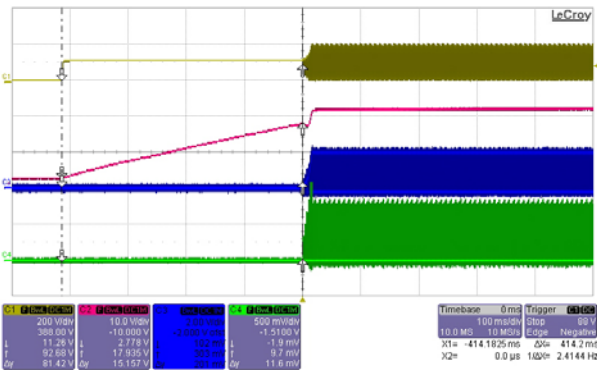


Figure 10 Constant charging VCC during startup

- Ch1 Drain source voltage
- Ch2 VCC supply voltage
- Ch3 Zero crossing voltage
- Ch4 Current sense voltage

Test condition: input 85Vac output 2.4A load


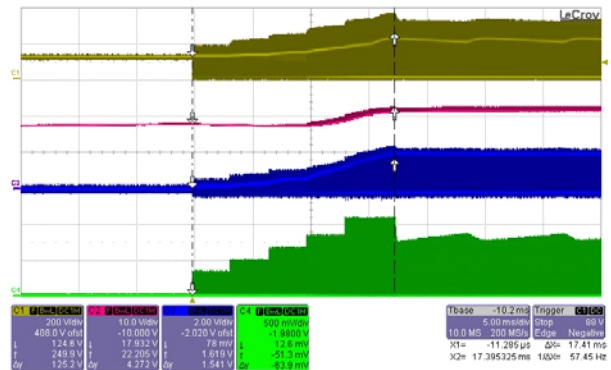


Figure 11 Softstart of current in 4 steps

- Ch1 Drain source voltage
- Ch2 VCC supply voltage
- Ch3 Zero crossing voltage
- Ch4 Current sense voltage


Test condition: input 85Vac output 2.4A load

### 12.2 Working at different zero crossing point

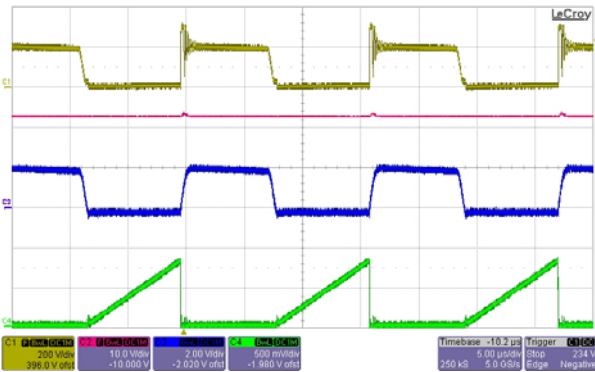

**Figure 12 Working at first ZC point**


Ch1 Drain source voltage  
 Ch2 VCC supply voltage  
 Ch3 Zero crossing voltage  
 Ch4 Current sense voltage  
 Test condition: 5V/2.4A @85Vac

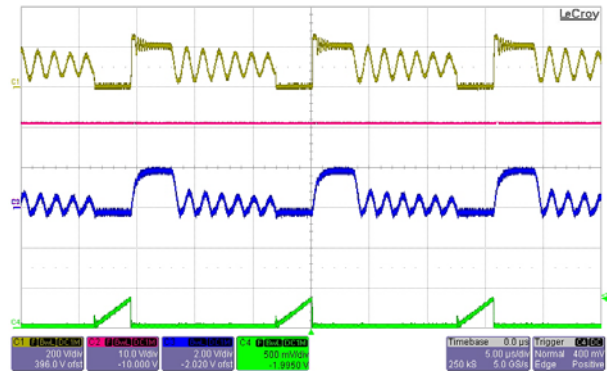

**Figure 13 Working at 7th ZC point**


Ch1 Drain source voltage  
 Ch2 VCC supply voltage  
 Ch3 Zero crossing voltage  
 Ch4 Current sense voltage  
 Test condition: 5V/0.5A @85Vac

### 12.3 Load transient response

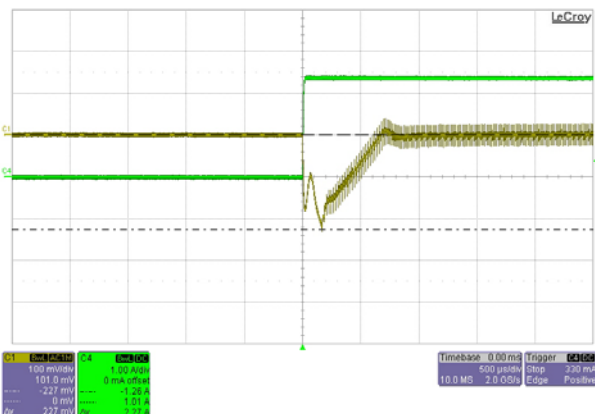

**Figure 14 AC output ripple undershoot**

Ch1 Output ripple voltage div 100mV  
 Ch4 Output current  
 Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz  
 Test condition: 0A to 2.4A

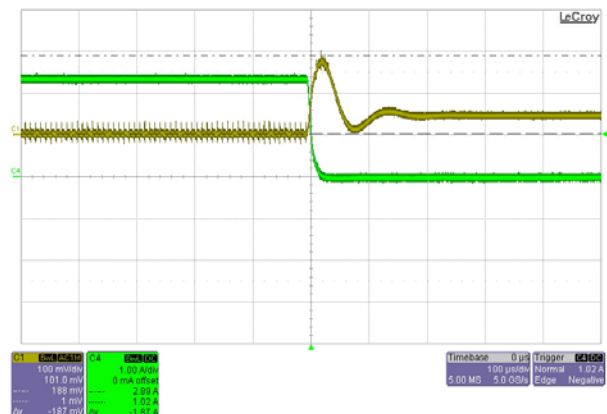


**Figure 15 AC output ripple overshoot**

Ch1 Output ripple voltage div 110mV  
 Ch4 Output current  
 Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz  
 Test condition: 2.4A to 0A



### 12.4 AC Output ripple during full load

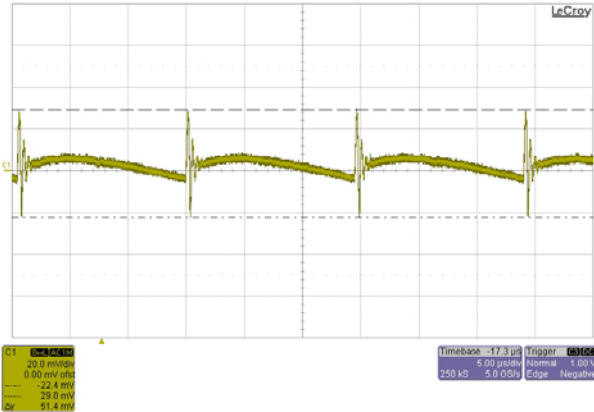


**Figure 16 AC output ripple at 85 Vac input**

Ch1 Output ripple voltage div 20mV

Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz

Test condition: 85V 5V/2.4A

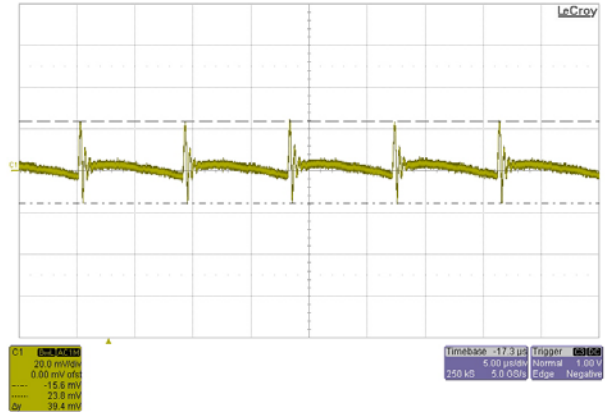


**Figure 17 AC output ripple at 265 Vac input**

Ch1 Output ripple voltage div 20mV

Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz

Test condition: 265V 5V/2.4A

### 12.5 Burst mode operation

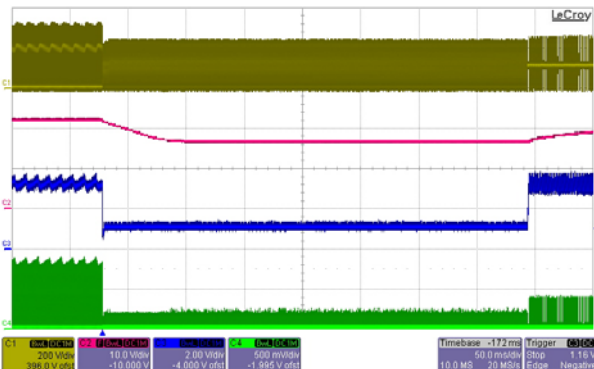

**Figure 18 Entering burst mode**


Ch1 Drain source voltage

Ch2 Supply voltage VCC

Ch3 Feedback voltage Vfb

Ch4 Current sense voltage

Test condition: load jump from 2.4A to 0.1A at 85Vac line

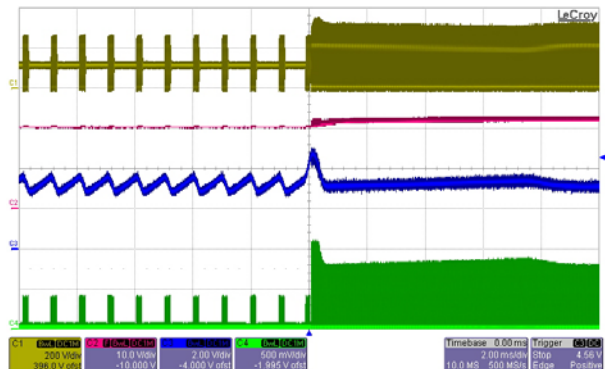

**Figure 19 Leaving burst mode**


Ch1 Drain source voltage

Ch2 Supply voltage VCC

Ch3 Feedback voltage Vfb

Ch4 Current sense voltage

Test condition: load jump from 0A to 2.4A at 85Vac line

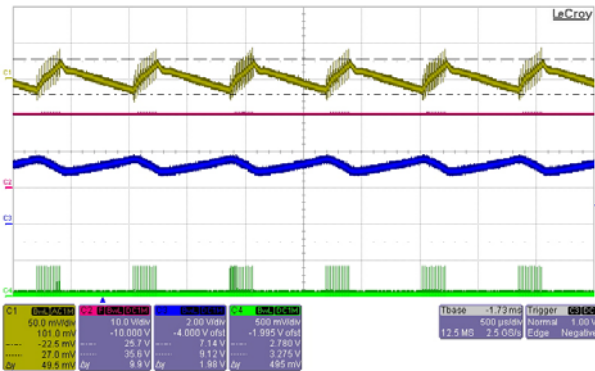
**Figure 20 AC output ripple during 85Vac**

Ch1 AC output ripple div 50mv


Ch2 Supply voltage VCC

Ch3 Feed back voltage VfB

Ch4 Current sense voltage

Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz

Test condition : 85V ac line, 5V/0.1A

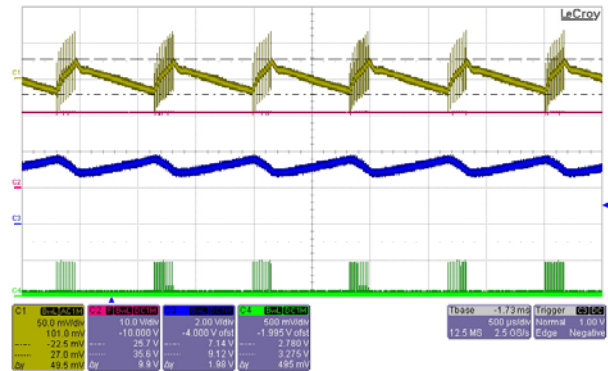
**Figure 21 AC output ripple during 265V**

Ch1 AC output ripple div 50mv

Ch2 Supply voltage VCC

Ch3 Feed back voltage VfB

Ch4 Current sense voltage

Measured with decouple capacitor 0.1uF+10uF, scope bandwidth 20MHz

Test condition : 265V ac line, 5V/0.1A

## 13 References

- [1] ICE2QR4765Z datasheet, Infineon Technologies AG, 2011
- [2] ICE2QS03G Design Guide Infineon Technologies AG,2010
- [3] Design Tips for flyback converters using the Quasi-Resonant (ANPS0005), Infineon Technologies AG, 2006
- [4] Converter Design Using the Quasi-Resonant PWM Controller ICE2QS01 (ANPS0003), Infineon Technologies AG, 2006
- [5] Determine the Switching Frequency of Quasi-Resonant Flyback Converters Designed with ICE2QS01 (ANPS0004), Infineon Technologies AG, 2006